

Layers of a Computing System

End-user


Application Software

System Software

Computer Architecture

Electronics, Gates and Circuits

Data Representation

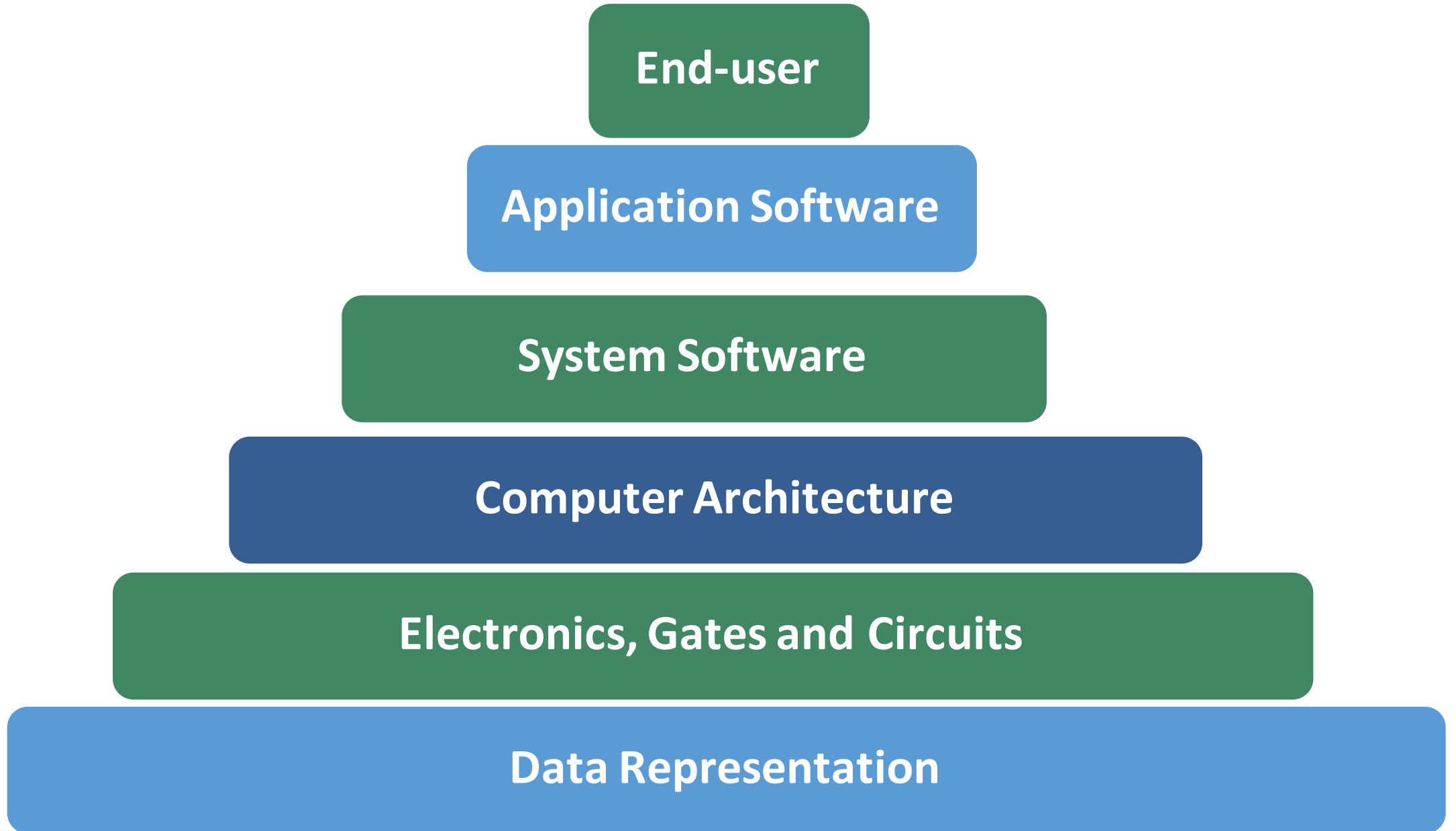

Data Representation

A Bit (Binary digit) has two possible values – 0 and 1

Used to represent one of two discrete states.

0 (OFF) or 1 (ON)

0 (False) or 1 (True)

Two bits can represent four different things.


Three bits can represent eight different things.

How many things can n bits represent?

Bits are used to represent numbers, text characters, images, sound, etc.

Binary (bit) Addition

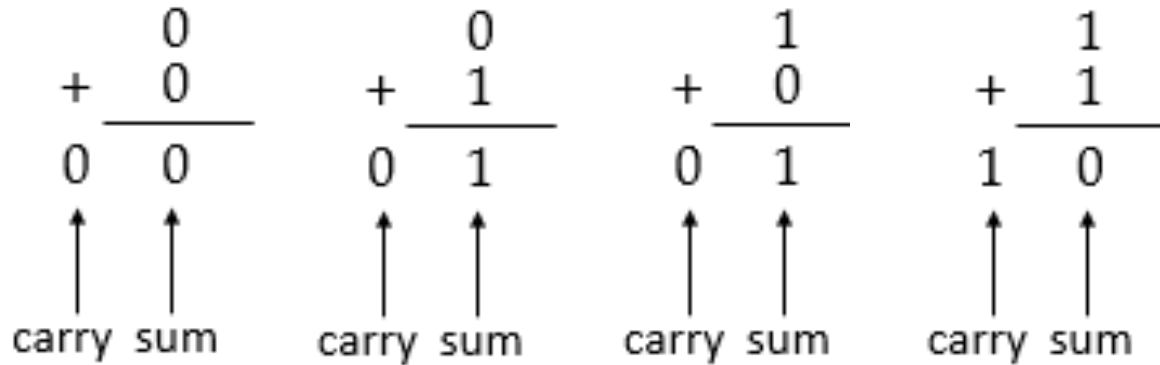Only four possible combinations of input:



A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


Truth Table

Boolean Expressions

$$SUM = A \cdot \bar{B} + \bar{A} \cdot B$$


$$CARRY = A \cdot B$$

Logic Gates (Circuit)

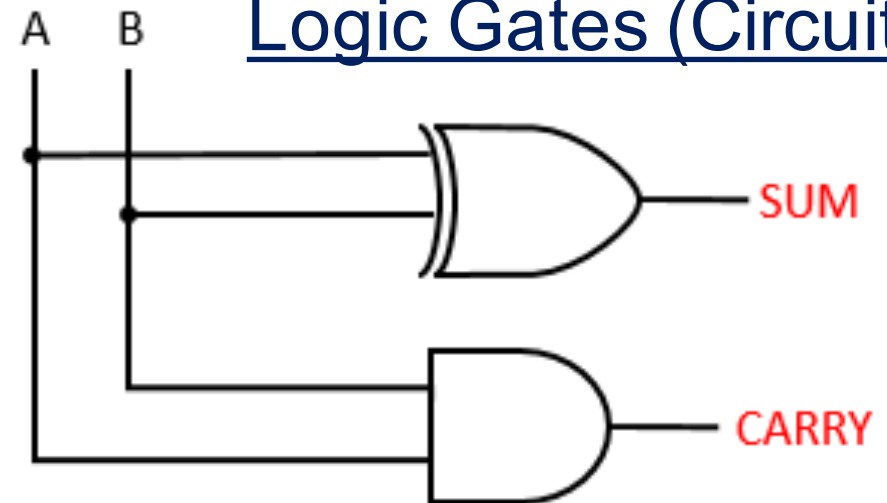

Logic Gates

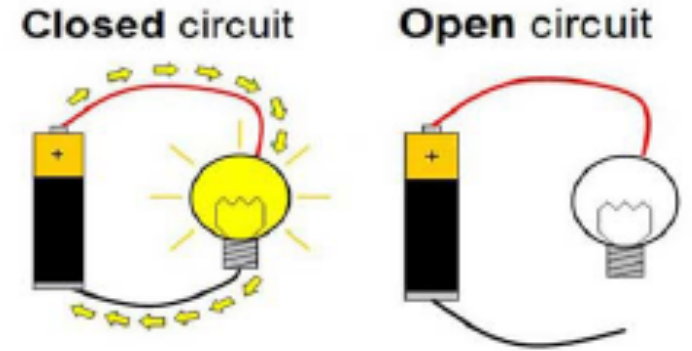Bits can be used to represent electrical signals:
0 (0V) or 1 (5V)



A gate is a device that performs a logical operation on electrical signals

These logical operations were defined by the mathematician George Boole (1815-64)


The most common logic (Boolean) operations are:

NOT
AND
OR


XOR
NAND
NOR

Logic Gates Symbols

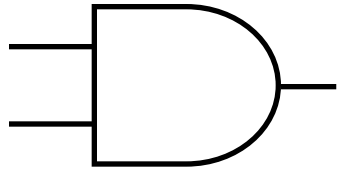
Each gate has its own logic symbol which allows circuits to be represented by a logic diagram




AND

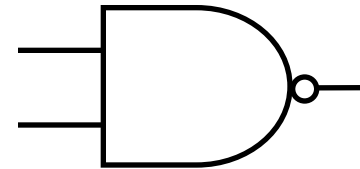


NAND

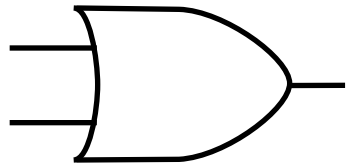


OR

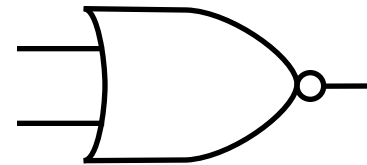

NOR

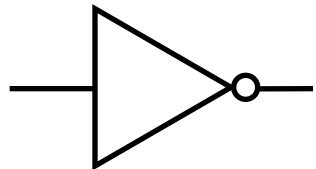

NOT

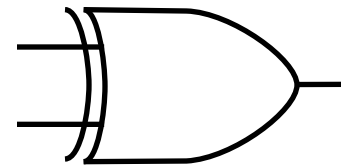

Exclusive OR (XOR)

Logic gates have one or more inputs and a single output

Logic Gates

The behaviour of gates (and circuits) are commonly represented in any of the following ways:

Boolean Expressions

Uses Boolean algebra, a mathematical notation for expressing two-valued logic

Logic Diagrams

A graphical representation of a circuit; each gate has its own symbol

Truth Tables

A table showing all possible input values and the associated output values

The AND operation




Logic Gate Symbol

A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

Truth Table

In order for the output to be 1 both inputs must be 1

The AND operation

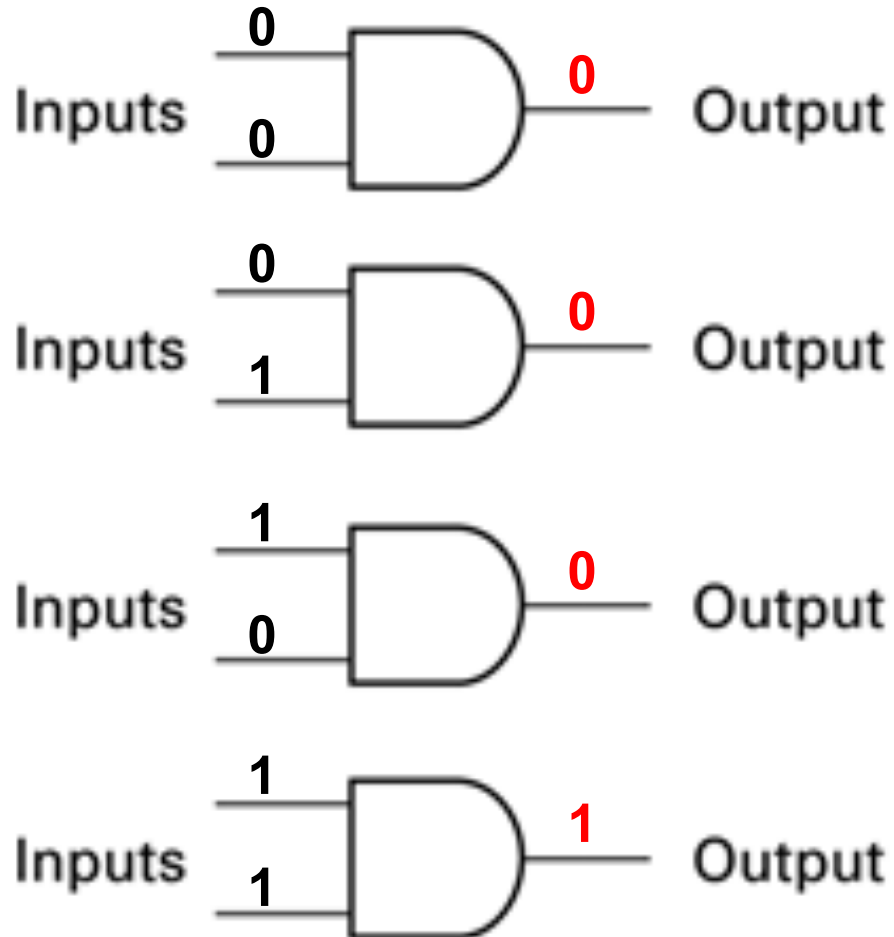

Truth Table

<u>Inputs</u>		<u>Output</u>
0	0	0
0	1	0
1	0	0
1	1	1

0 = FALSE

1 = TRUE

AND operation

- Both input values must be TRUE for output to be TRUE

The OR operation




Logic Gate Symbol

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

Truth Table

In order for the output to be 1 either input must be 1.

The NOT operation

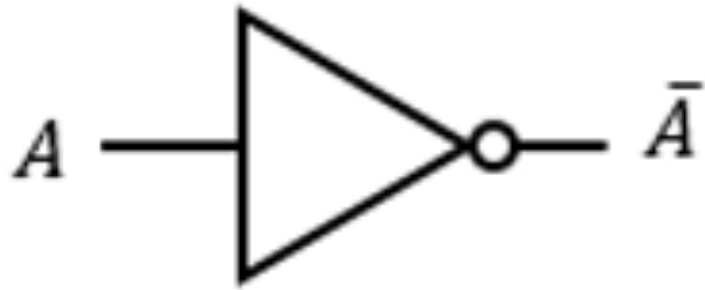


Logic Gate Symbol

A	\bar{A}
0	1
1	0

Truth Table

Inverts a single input. Also called an inverter.

NAND

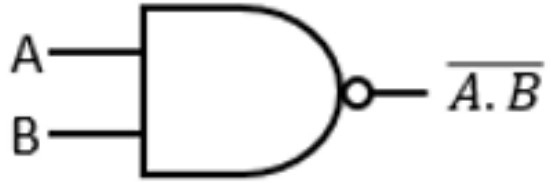


Logic Gate Symbol

A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table

$$A \text{ NAND } B = \text{NOT } (A \text{ AND } B)$$

NOR

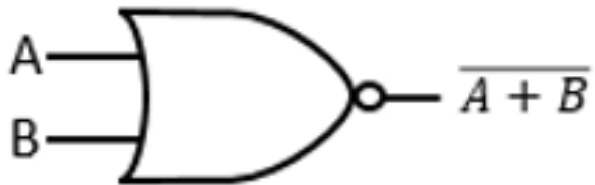


Logic Gate Symbol

A	B	$\overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

Truth Table

$$A \text{ NOR } B = \text{NOT } (A \text{ OR } B)$$

The XOR (eXclusive OR) operation

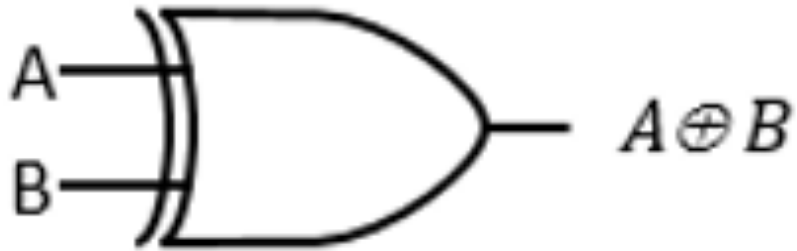

Logic Gate Symbol

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	0

Truth Table

In order for the output to be 1 either (but not both) inputs must be 1.

$$(A \text{ AND NOT } B) \text{ OR } (\text{NOT } A \text{ AND } B) = A \text{ XOR } B$$

Boolean Algebra

Boolean Constants: these are '0' (false) and '1' (true)

Boolean Variables: variables that can only take the values '0' or '1'

Boolean Functions: such as NOT, AND and OR (in that order)

Boolean Theorems: a set of identities and laws

Law	AND	OR
Commutative	$A \cdot B = B \cdot A$	$A + B = B + A$
Associative	$A \cdot (B \cdot C) = (A \cdot B) \cdot C$	$A + (B + C) = (A + B) + C$
Absorption	$A \cdot (A + B) = A$	$A + (A \cdot B) = A$
Distributive	$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$	$A + (B \cdot C) = (A + B) \cdot (A + C)$
De Morgan's Law	$\overline{A \cdot B} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A} \cdot \bar{B}$

Complete the truth table for a Boolean expression

$$A + \bar{B}$$

A	B
0	0
0	1
1	0
1	1

\bar{B}
1
0
1
0

$A + \bar{B}$
1
0
1
1

Complete the truth table for a Boolean expression

$\overline{A.B}$

A	B	A.B	$\overline{A.B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

Using truth tables to verify identities

Let's say we wanted to investigate whether the identity holds

A	B	\bar{A}	\bar{B}	$\bar{A} \cdot \bar{B}$	A.B	$\overline{A \cdot B}$
0	0	1	1	1	0	1
0	1	1	0	0	0	1
1	0	0	1	0	0	1
1	1	0	0	0	1	0

Is NOT A AND NOT B = NOT (A AND B) ?

Using truth tables to verify identities

Investigate whether the identity holds

$$A + (A \cdot B) = A$$

A	B	A · B	A + (A · B)
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

Using truth tables to verify identities

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

$B + C$	$A \cdot (B + C)$
0	0
1	0
1	0
1	0
0	0
1	1
1	1
1	1

$A \cdot B$	$A \cdot C$	$(A \cdot B) + (A \cdot C)$
0	0	0
0	0	0
0	0	0
0	0	0
0	0	0
0	1	1
1	0	1
1	1	1

Distribution : $A \cdot (B + C) = (A \cdot B) + (A \cdot C)$

Using truth tables to verify identities

A	B	C	B.C	$A + (B.C)$	$A + B$	$A + C$	$(A + B).(A + C)$
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1


Distribution : $A + (B.C) = (A + B).(A + C)$

Using truth tables to verify identities - exercise


De Morgan's laws are used to simplify Boolean equations so that you can build equations only involving one sort of gate.

Verify De Morgan's laws using truth tables
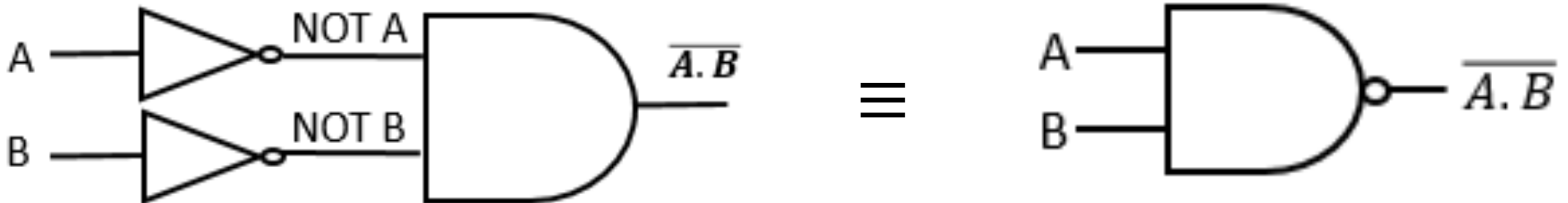
$$\bar{A} + \bar{B} = \overline{A \cdot B}$$


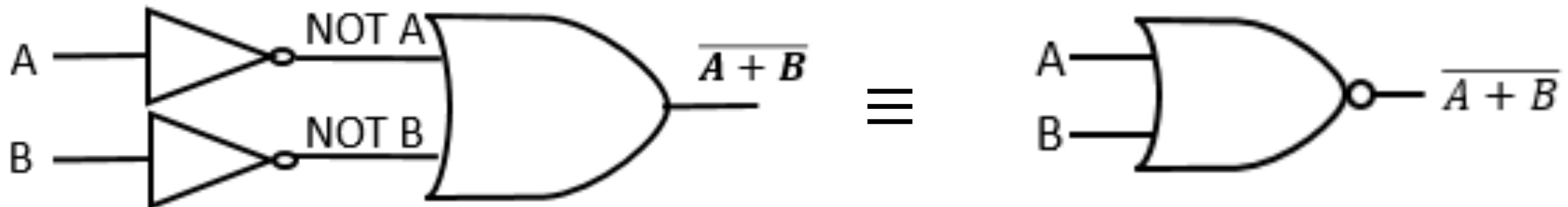
$$\bar{A} \cdot \bar{B} = \overline{A + B}$$



Using truth tables to verify identities - SOLUTIONS

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$


A	B	$A \cdot B$	$\overline{A \cdot B}$	\bar{A}	\bar{B}	$\bar{A} + \bar{B}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

A	B	$A + B$	$\overline{A + B}$	\bar{A}	\bar{B}	$\bar{A} \cdot \bar{B}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0


Create a Boolean Expression from a logic diagram

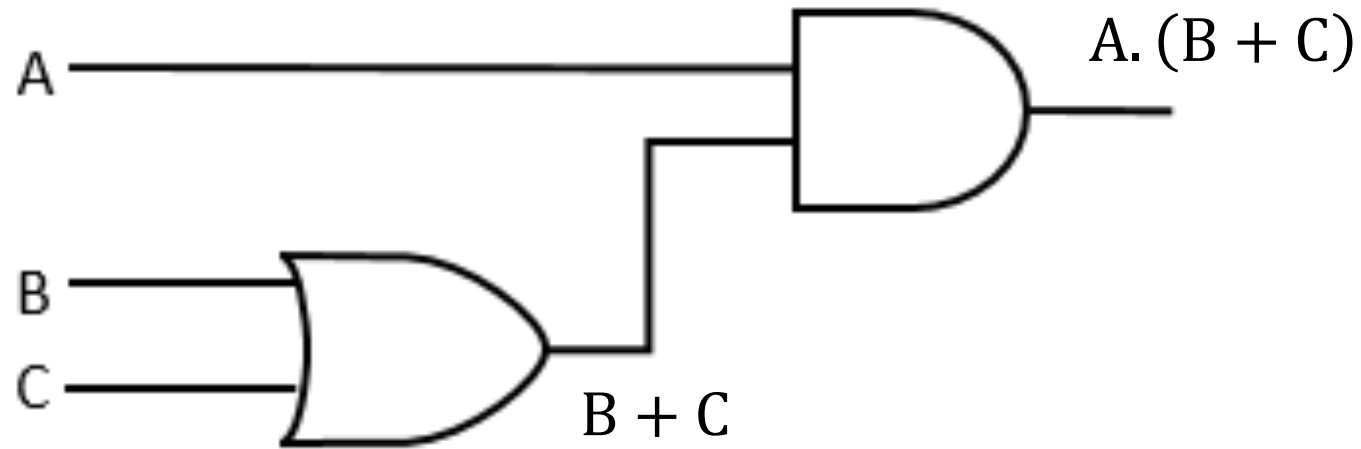Work progressively from the inputs to the output adding logic expressions to the output of each gate in turn







Create a Boolean Expression from a logic diagram

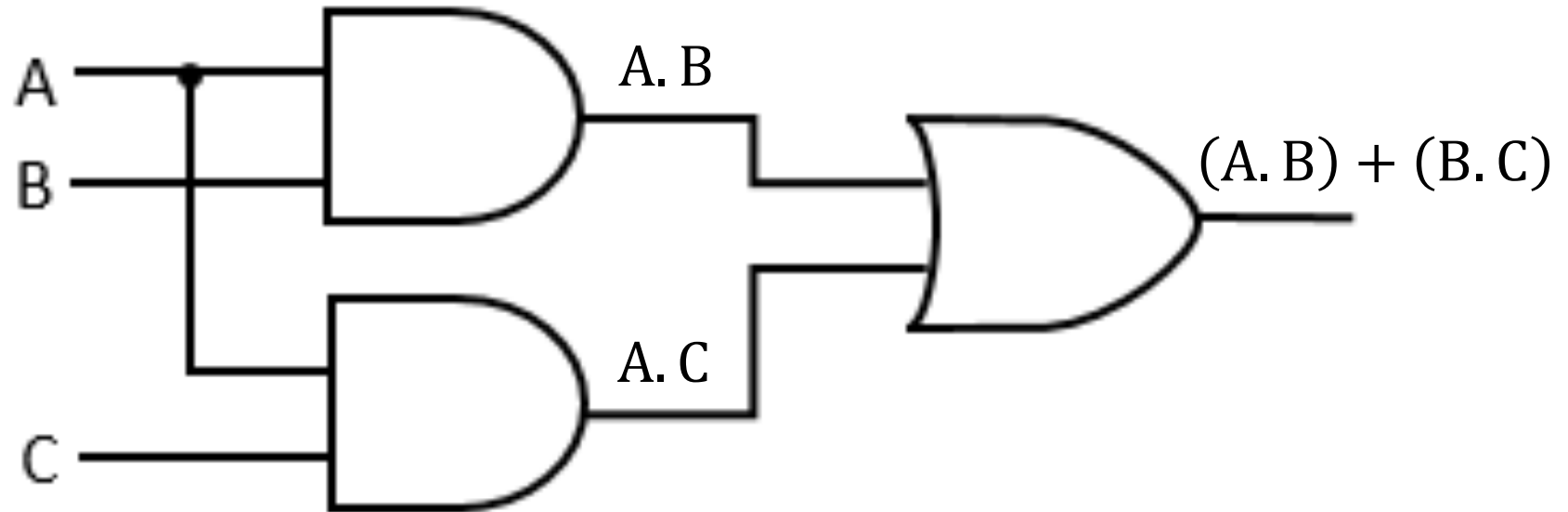Work progressively from the inputs to the output adding logic expressions to the output of each gate in turn



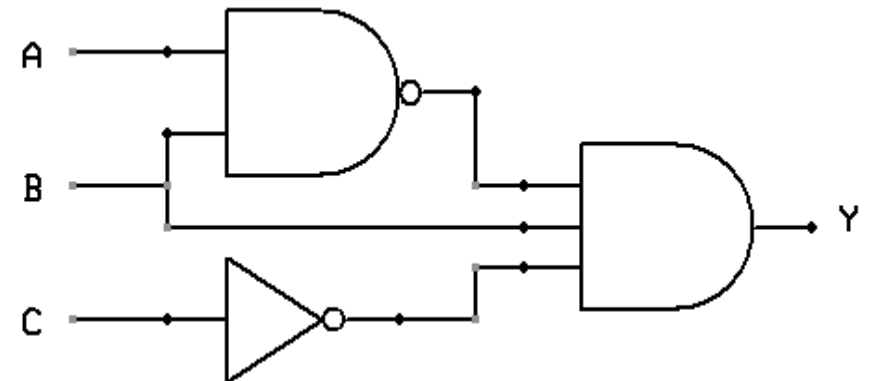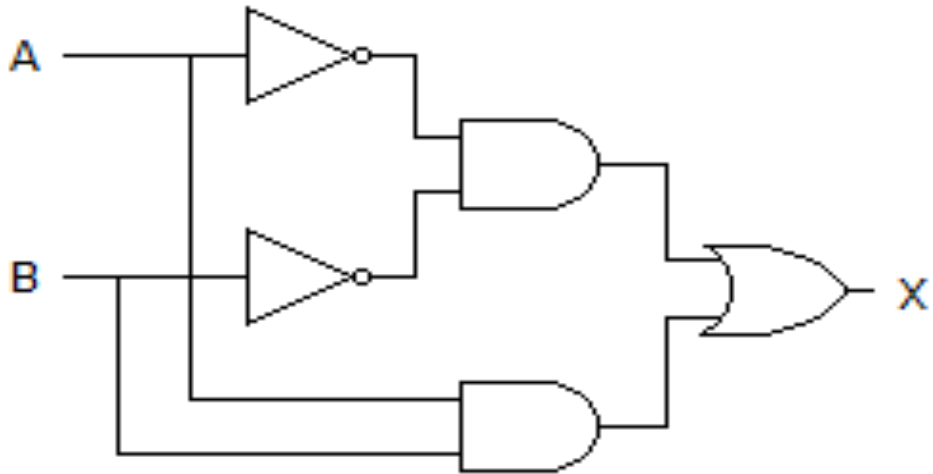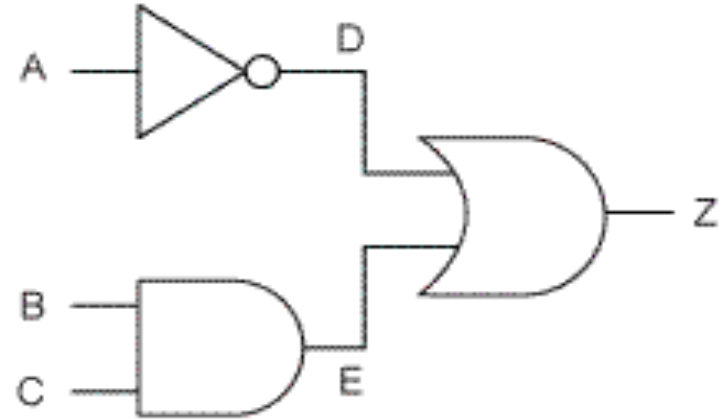
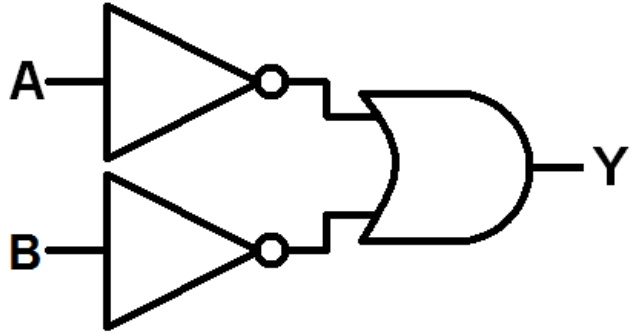
Create a Boolean Expression from a logic diagram



Connect Logic Gates (to create circuits)


Logic gates may be combined by using the output of one gate as the input to another.

A	B	A OR B	Q = NOT (A OR B)	A NOR B
0	0	0	1	1
0	1	1	0	0
1	0	1	0	0
1	1	1	0	0

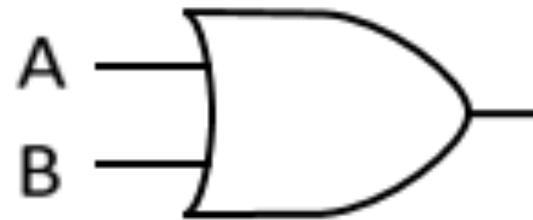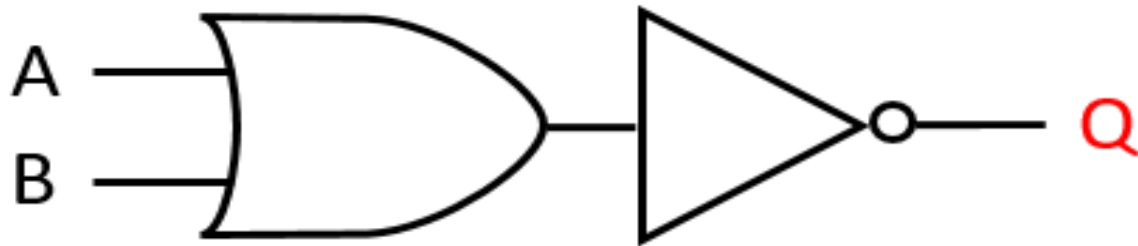

Connect Logic Gates (to create circuits)

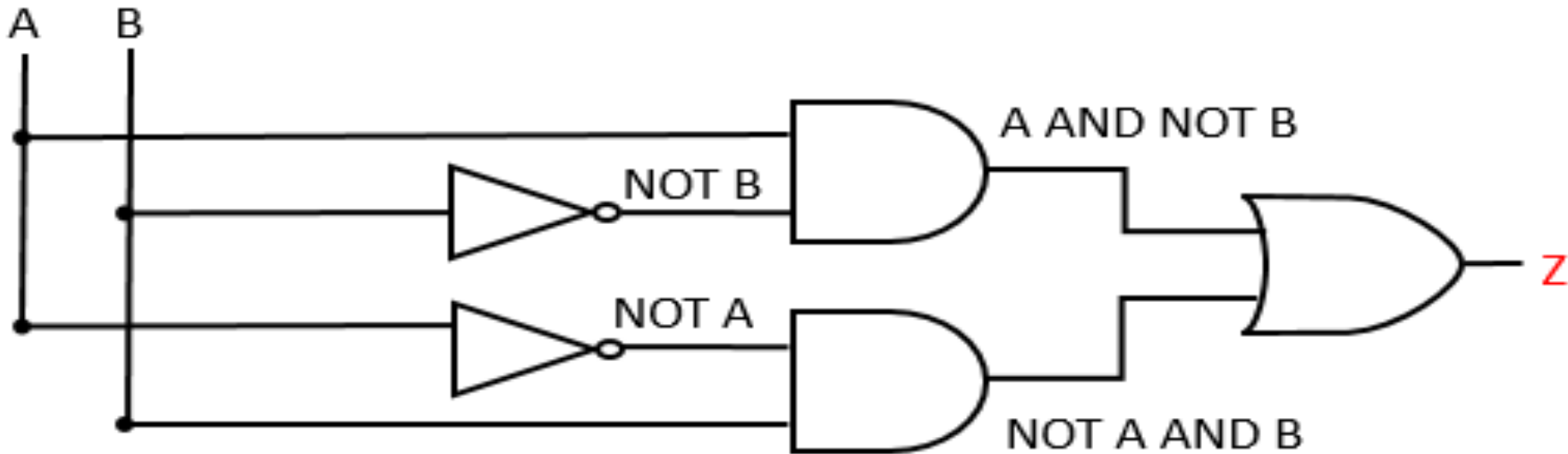Circuits in which the output is determined solely by the current inputs are termed **combinational logic circuits**.




A AND NOT B OR NOT A AND B = A XOR B



Half-adder


An adder is a digital circuit that performs addition of numbers.

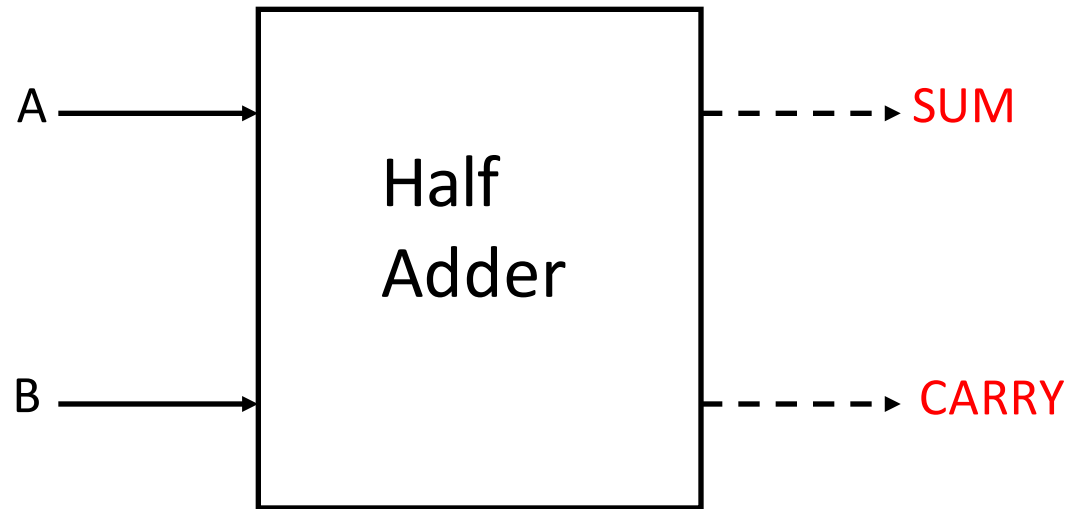A half adder adds two binary digits and produces two outputs – the sum and the carry



Half-adder

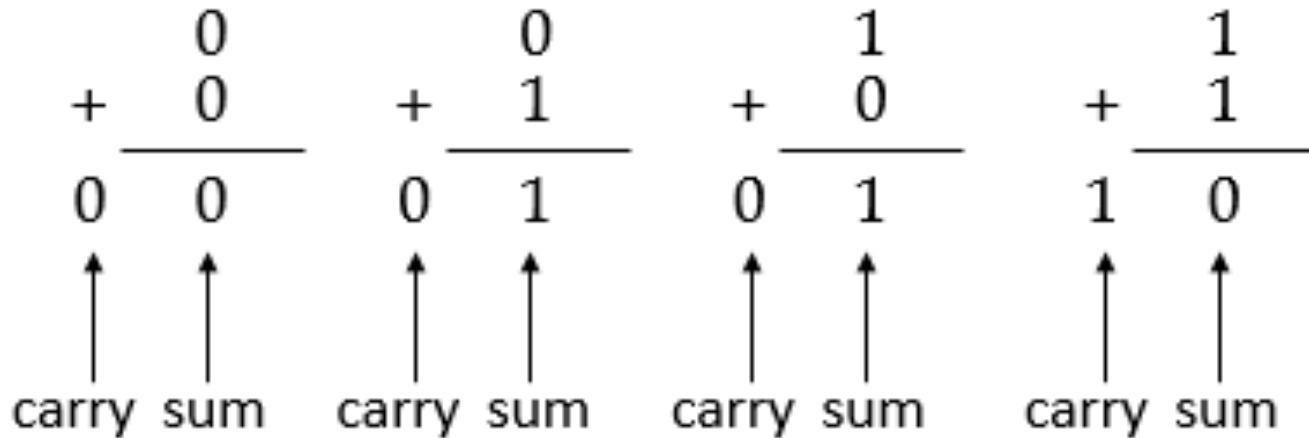Only four possible combinations of input:




$$SUM = A.\bar{B} + \bar{A}.B$$

$$CARRY = A.B$$


A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Half-adder

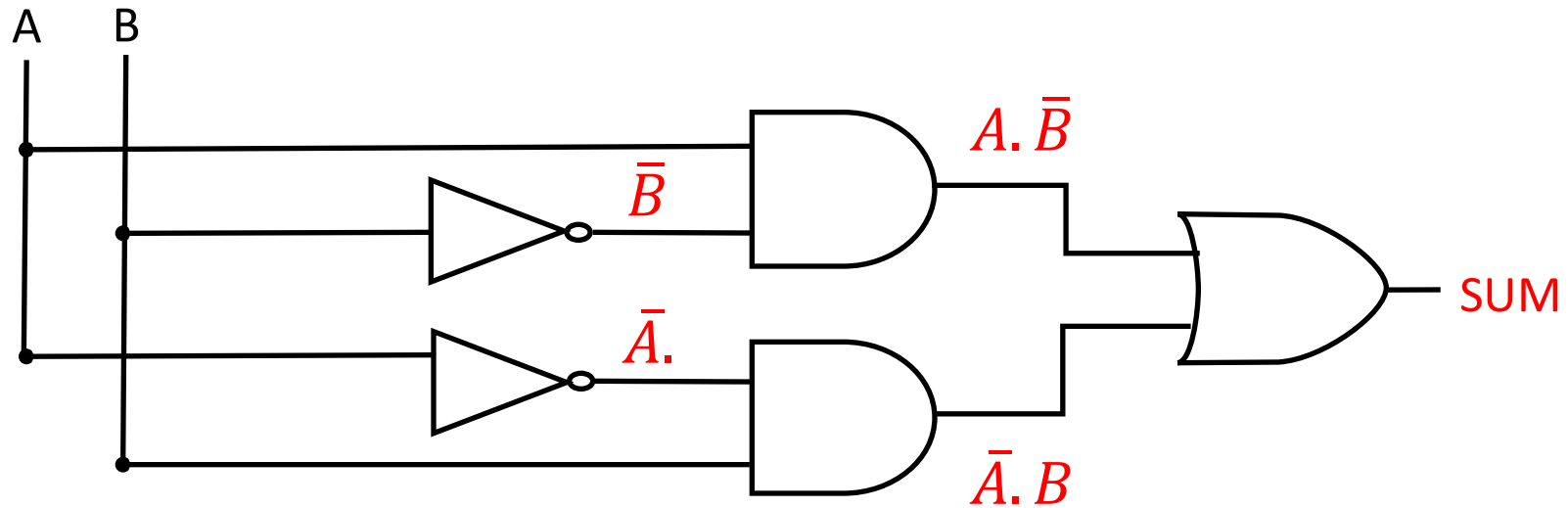
$$SUM = A \cdot \bar{B} + \bar{A} \cdot B$$



$$CARRY = A \cdot B$$

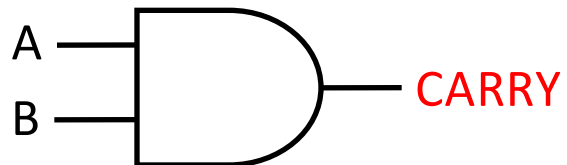

Half-adder

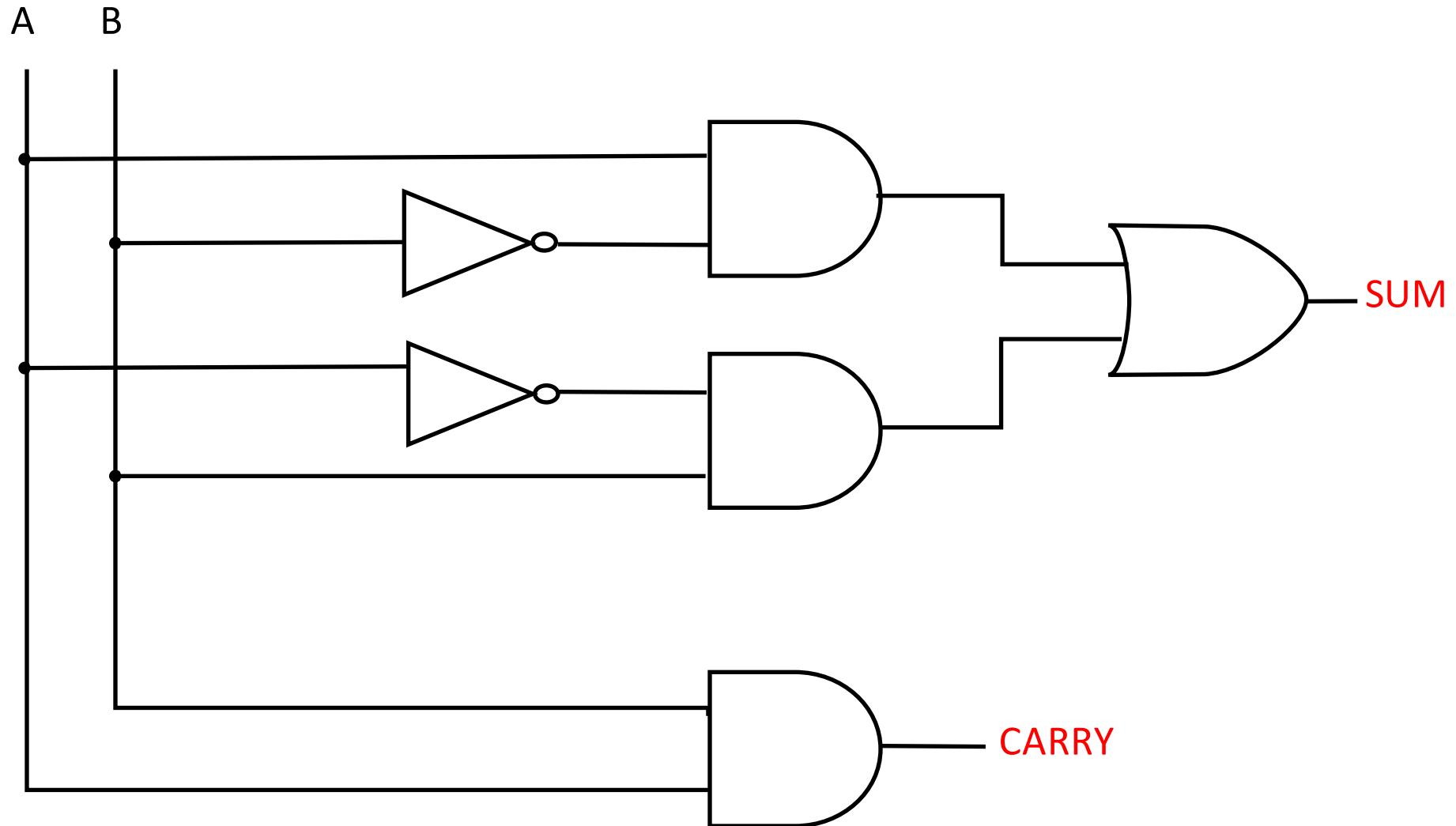


Half-adder (refined)

The circuit for SUM can be simplified as follows:


$$\begin{aligned} SUM &= A.\bar{B} + \bar{A}.B \\ &= A \oplus B \quad (\text{i.e. A XOR B}) \end{aligned}$$

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

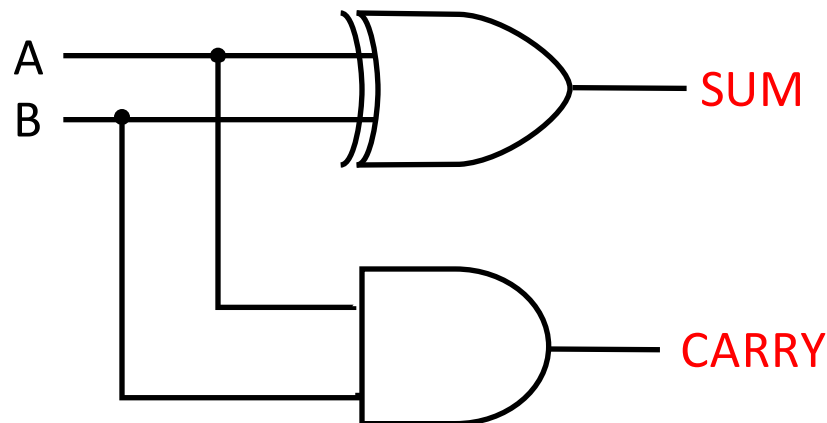The half-adder can now be realised with fewer gates as shown




Half-adder (operation)

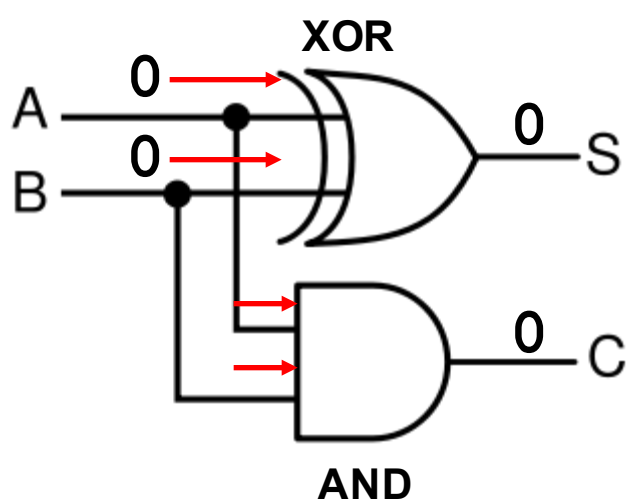


Inputs	Output
0 0	0
0 1	1
1 0	1
1 1	0

Inputs	Output
0 0	0
0 1	0
1 0	0
1 1	1

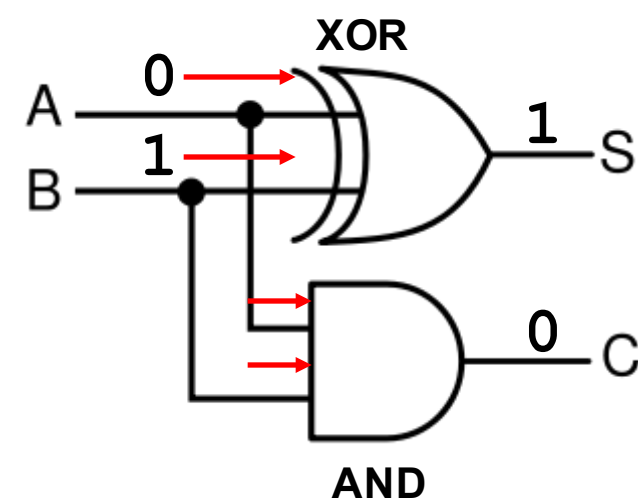


Inputs	Output
0 0	0
0 1	1
1 0	1
1 1	0

Inputs	Output
0 0	0
0 1	0
1 0	0
1 1	1

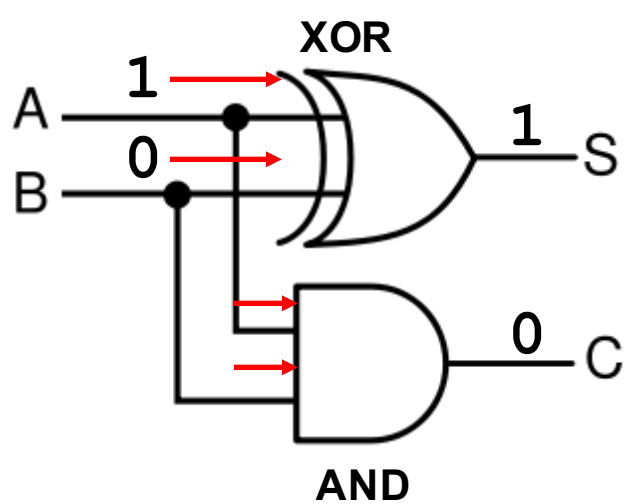

Inputs	Output
0 0	0
0 1	1
1 0	1
1 1	0

Inputs	Output
0 0	0
0 1	0
1 0	0
1 1	1

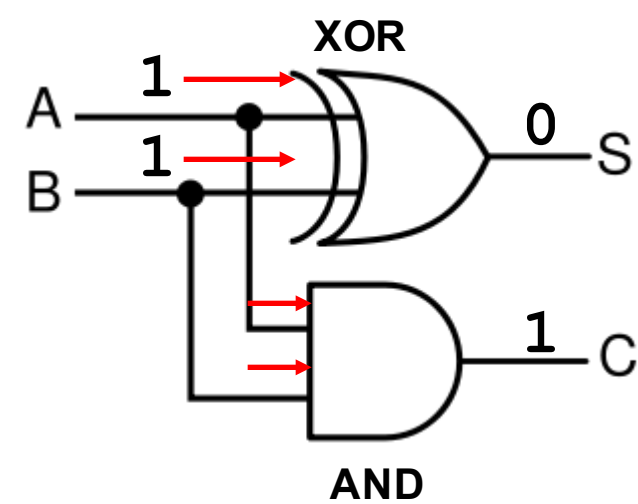


Inputs	Output
0 0	0
0 1	1
1 0	1
1 1	0

Inputs	Output
0 0	0
0 1	0
1 0	0
1 1	1

Full-adder

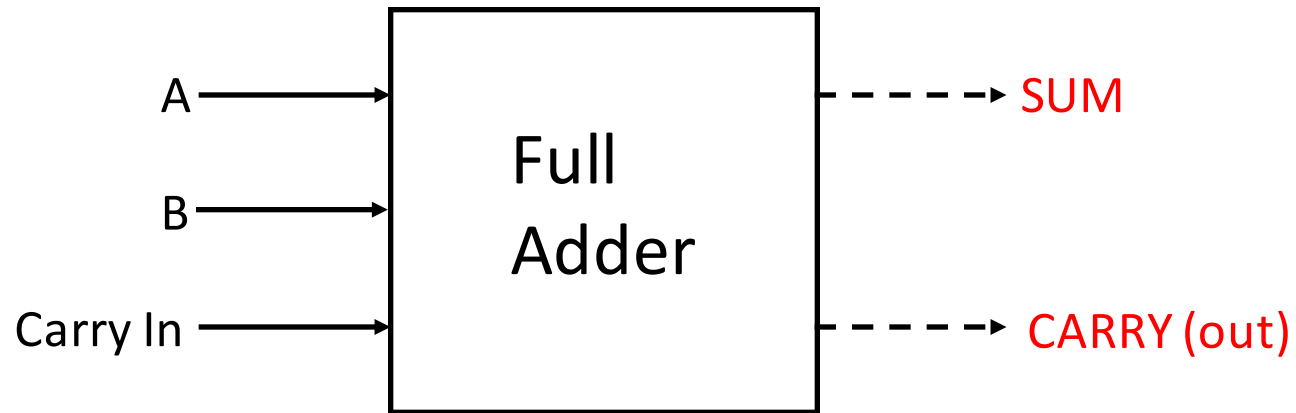A full adder adds the carry in bit to two binary digits and produces two outputs – the sum and carry out.



Full-adder

A full adder adds the carry in bit to two binary digits and produces two outputs – the sum and carry out

A	B	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$SUM = \bar{A}.\bar{B}.C + \bar{A}.B.\bar{C} + A.\bar{B}.\bar{C} + A.B.C$$

$$CARRY = \bar{A}.B.C + A.\bar{B}.C + A.B.\bar{C} + A.B.C$$

Full-adder *(circuit for SUM)*

$$SUM = \bar{A}.\bar{B}.C + \bar{A}.B.\bar{C} + A.\bar{B}.\bar{C} + A.B.C$$

$$SUM = \bar{A}(\bar{B}.C + B.\bar{C}) + A(\bar{B}.\bar{C} + B.C)$$

Taking,

$$X = B \oplus C$$


$$\bar{B}.\bar{C} + B.C = \overline{B \oplus C}$$

$$\bar{B}.C + B.\bar{C} = B \oplus C$$

$$SUM = \bar{A}.X + A.\bar{X}$$

$$SUM = A \oplus X$$

$$SUM = A \oplus B \oplus C$$

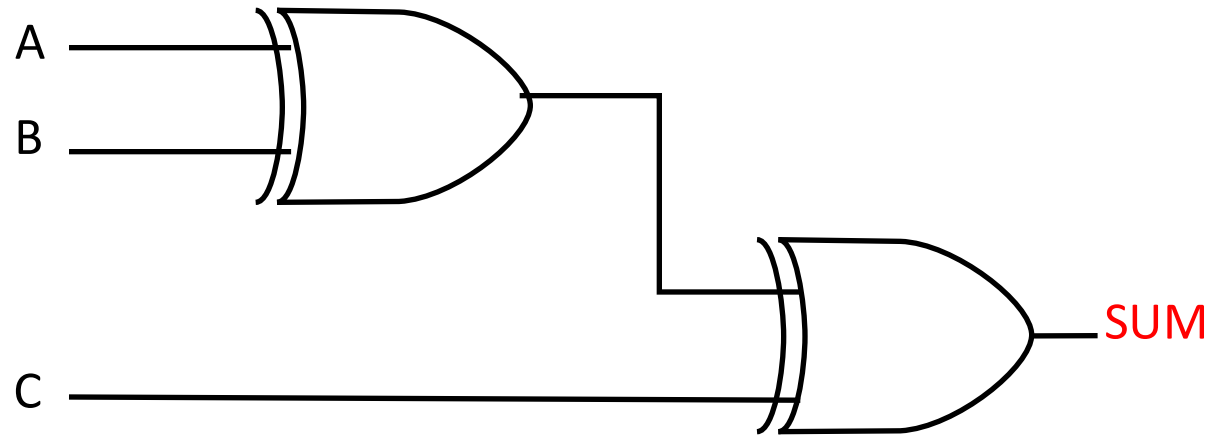


Full-adder *(circuit for CARRY)*

$$CARRY = \bar{A}.B.C + A.\bar{B}.C + A.B.\bar{C} + A.B.C$$

$$CARRY = C(\bar{A}.B + A.\bar{B}) + A.B(C + \bar{C})$$

$$CARRY = C(A \oplus B) + A.B$$

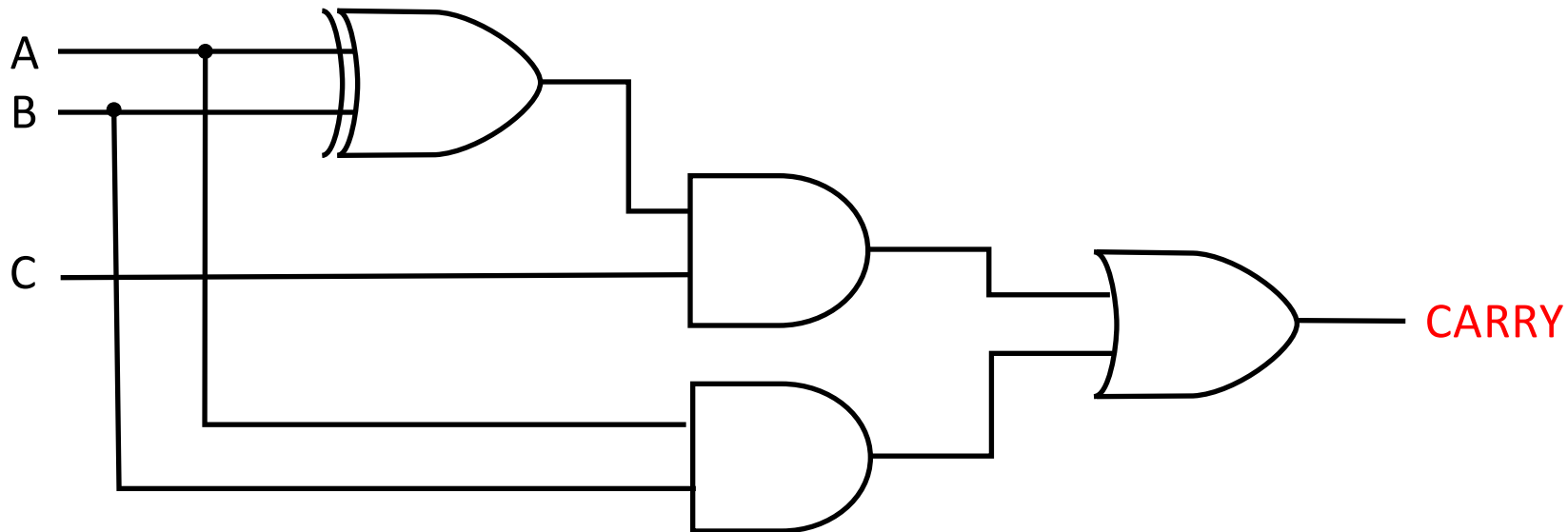

Full-adder

$$SUM = A \oplus B \oplus C$$

$$CARRY = C.(A \oplus B) + A.B$$

